Making the simplest Transmitter

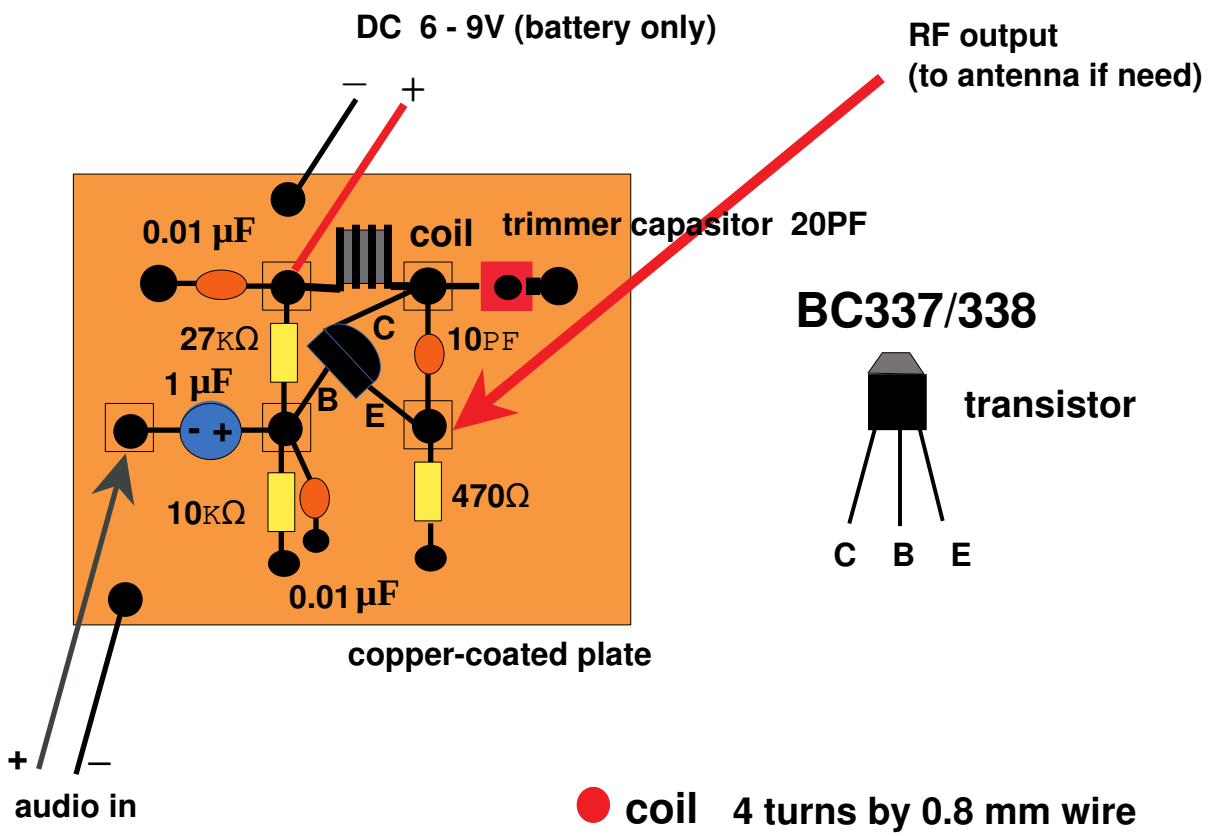

- coil 4 turns by 0.8 mm wire
  5mm diameter

- registers
  - 470 Ω *(yellow-violet-brown)*
  - 10K Ω *(brown-black-orange)*
  - 27K Ω *(red-violet-orange)*
- capacitors
  - 10 PF
  - 0.01µF *(103)*
  - 1 µF
- trimmer capasitor 20PF

- soldered point:
  - : direct to the ground

  - : insulated from the ground

2023-09-14 by Tetsuo Kogawa